

Lab 1

Task 1

Simulating a basic 8-bit binary counter

```
module counter #( //file name and module name must be the same
    parameter WIDTH = 8 // specify counter bit width
)(
    //interface signals
    input logic      clk, //clock
    input logic      rst, //reset
    input logic      en, //counter enable
    output logic [WIDTH-1:0] count //count output
);

//always_ff specifies a clocked circuit. This is an asynchronous reset
always_ff @ (posedge clk, posedge rst)
    if (rst) count <= {WIDTH{1'b0}}; //non-blocking assignment (asynchronous).
    // { } is used to form WIDTH bits of 0
    else count <= count + {{WIDTH-1{1'b0}}, en};

endmodule
```

Note that we use '<=', which is a non-block assignment as it means that all registers would be updated simultaneously on the clock edge and not sequentially

Additionally, note that the concatenation operator { } creates (WIDTH-1) number of zeros, and is constructed with en, effectively extending en (1 bit) to match WIDTH bits.

```

/*
Mandatory header files.
Note the name Vcounter.h is for the module counter
*/

#include "Vcounter.h"
#include "verilated.h"
#include "verilated_vcd_c.h"

int main(int argc, char **argv, char **env) {
    int i; // counts the number of clock cycles to simulate
    int clk; //clk is the module clock signal

    Verilated::commandArgs(argc, argv);
    //Instantiate the counter module as Vcounter.This is the DUT
    Vcounter* top = new Vcounter;

    /*
    initialise trace dump
    Turn on signal tracing, and tell verilator to dump the waveform data
    to counter.vcd file
    */

    Verilated::traceEverOn(true);
    VerilatedVcdC* tfp = new VerilatedVcdC;
    top->trace(tfp, 99);
    tfp->open("counter.vcd");

    /*
    Initialise simulation inputs
    Sets initial signal values before simulation
    Top is the name of the top-level entity
    Only the top-level signals are visible
    */

```

```
top→clk = 1;  
top→rst = 1;  
top→en = 0;
```

```
/*  
run simulation for many clock cycles
```

The for loop is where the simulation happens
i counts the clock cycles

```
*/  
for (i=0; i<300; i++){  
    //change rst and en signls during simulation. rst = 1 for i = 0, 1, 15. rst = 0  
for all other cycles  
    top →rst = (i < 2) | (i==15);  
    top → en = (i > 4); //en turns on from i = 5 onwards
```

```
  
    //dump variables into VCD file and toggle clock  
    for (clk=0; clk<2; clk++){  
        // time is in ps. tfp is responsible for for recording all values  
        // during the simulation  
        tfp→dump(2*i+clk);  
        top→clk = !top→clk; //toggle clock  
        top→eval(); //evaluate model again with new clock value  
    }  

```

```
/*  
shifted by 1 as rst and en code block is after the for loop.  
Therefore, evaluation of the clock is done before the reset and enable is  
evaluated again  
*/
```

```
  
if (Verilated::gotFinish()) exit(0); //exit if finish signal received  
  
}
```

```

tfp → close(); //close VCD file
exit(0); //exit program
}


```

Note that time is in ps as most clocks are in MHz - GHz range, so picosecond resolution helps ensure accurate edge alignment.

However, the time axis's unit does not matter as the circuit is clock-based, not time-based

Moreover, time is in ps because Verilator uses ps as the default time unit


GTK wave output

 


Test yourself challenges:

1. Modify the testbench so that you stop counting for 3 cycles once the counter reaches 0x9, and then resume counting. You may also need to change the stimulus for *rst*.
 - a. You just need to modify the *en* and *rst* values in the for loop in the testbench (modify 'i')
2. The current counter has a synchronous reset. To implement asynchronous reset, you can change line 11 of counter.sv to detect change in *rst* signal. (See notes.)\

 - a. Change the counter.sv code to "always_ff @ (posedge clk, posedge rst)" instead to look for a positive edge in rst. There is a slight bug in Verilog with the implementation of asynchronous reset, where it doesn't reset instantly. This is why asynchronous functions are avoided. The bug may be due to the fact that res changes on clock cycle, which usually never happens.
3. Make these modifications, compile, and run. Examine the waveform with GTKwave and explain what you see.
 - a. You can see from the GTK wave that en=1 on the 5th clock poscycle (i=0, i=1...). The count then increases on the next clock cycle when en=1.



The asynchronous bug is as follows, where reset happens the next half cycle

 

Task 2

Linking Verilator simulation with Vbuddy

```
/*
Mandatory header files.
Note the name Vcounter.h is for the module counter
*/

#include "Vcounter.h"
#include "verilated.h"
#include "verilated_vcd_c.h"
```

```

#include "vbuddy.cpp" // include vbuddy code

int main(int argc, char **argv, char **env) {
    int i; // counts the number of clock cycles to simulate
    int clk; //clk is the module clock signal

    Verilated::commandArgs(argc, argv);
        // Instantiate the counter module as Vcounter. This is the DUT
    Vcounter* top = new Vcounter;

    /*
    initialise trace dump
    Turn on signal tracing, and tell verilator to dump the waveform data
    to counter.vcd file
    */

    Verilated::traceEverOn(true);
    VerilatedVcdC* tfp = new VerilatedVcdC;
    top->trace(tfp, 99);
    tfp->open("counter.vcd");

    //init vbuddy
    if (vbdOpen()!=1) return(-1);
    vbdHeader("Lab 1: Counter");

    /*
    Initialise simulation inputs
    Sets initial signal values before simulation
    Top is the name of the top-level entity
    Only the top-level signals are visible
    */
    top->clk = 1;
    top->rst = 1;

```

```
top→en = 0;
```

```
/*
```

```
run simulation for many clock cycles
```

The for loop is where the simulation happens

i counts the clock cycles

```
*/
```

```
for (i=0; i<300; i++){
```

```
    // change rst and en signals during simulation.
```

```
    // rst = 1 for i = 0, 1, 15. rst = 0 for all other cycles
```

```
    top →rst = (i < 2) | (i==15);
```

```
    top→en = vbdFlag(); //en turns on when the button on vbuddy is pressed
```

```
    //dump variables into VCD file and toggle clock
```

```
    for (clk=0; clk<2; clk++){
```

```
        tfp→dump(2*i+clk);
```

```
        //time is in ps.
```

```
        //tfp is responsible for recording all values during the simulation
```

```
        top→clk = !top→clk; //toggle clock
```

```
        top→eval(); //evaluate model again with new clock value
```

```
    }
```

```
/*
```

```
//display count value on vbuddy
```

```
vbdHex(4, (int(top→count) >> 16) & 0xF);
```

```
vbdHex(3, (int(top→count) >> 8) & 0xF);
```

```
vbdHex(2, (int(top→count) >> 4) & 0xF);
```

```
vbdCycle(i+1); //display cycle number
```

```
*/
```

```
vbdPlot(int(top→count), 0, 255); //plot count value on vbuddy display
```

```
/*
```

```
shifted by 1 as rst and en code block is after the for loop.
```

Therefore, evaluation of the clock is done before the reset
and enable is evaluated again

*/

if (Verilated::gotFinish()) exit(0); //exit if finish signal received

}

vbdClose(); //close vbuddy

tfp → close(); //close VCD file

exit(0); //exit program

}